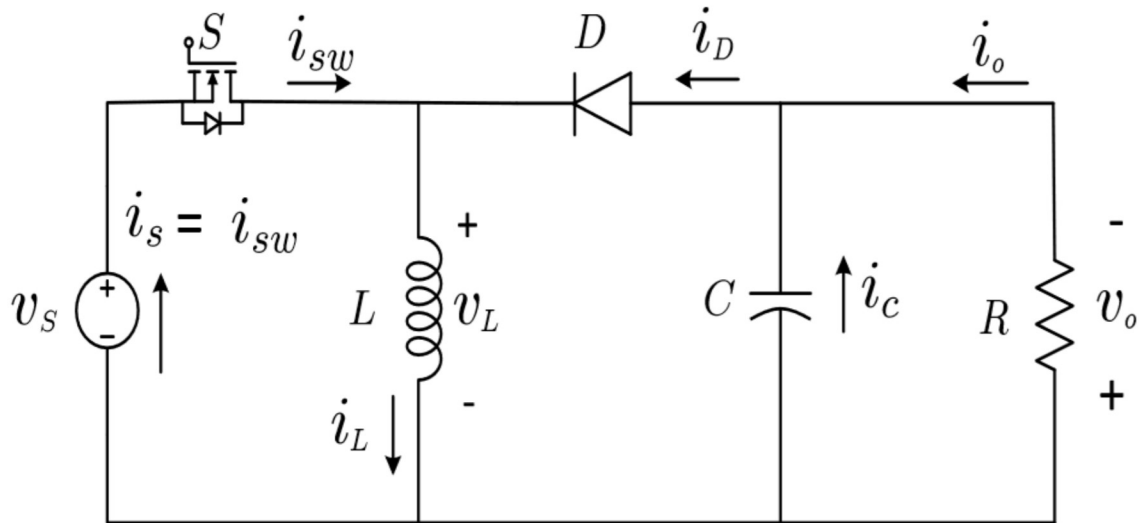


## BUCK-BOOST CONVERTER

**Definition:** Buck-Boost converter is a converter which can step up and down the output voltage compared to input source voltage.


**Circuit Diagram:**




**Designed Circuit Parameters:**

Parameters	Values
$V_s$	100 V
$D$	0.33
$L$	1.04 mH
$C$	6.67 mF
$R$	12.5 $\Omega$
$V_o$	50 V
$f$	40 KHz


Simulated Circuit:

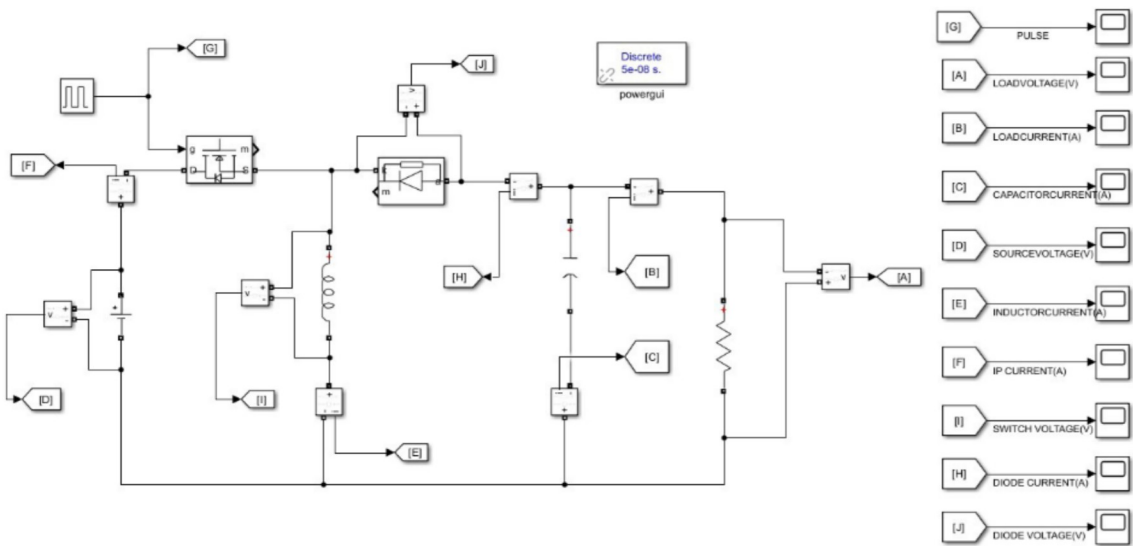


Simulated Output Results:

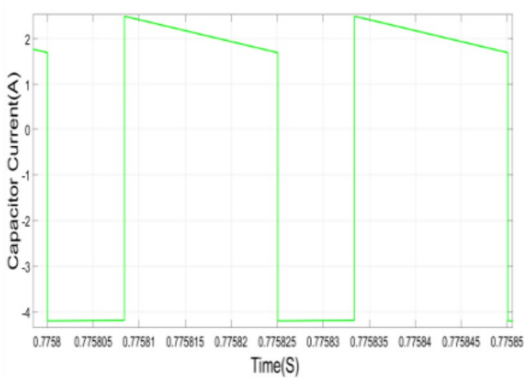


(a) figure 1

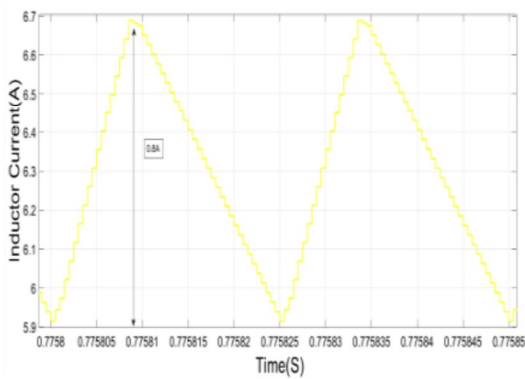


(b) figure 2

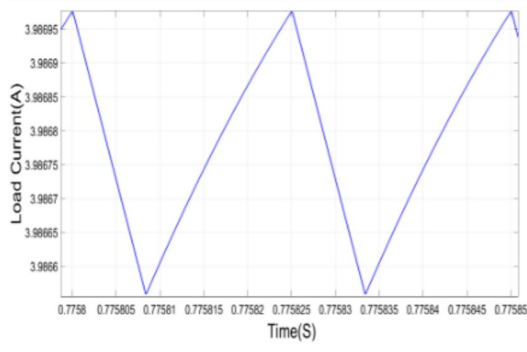


(a) figure 3

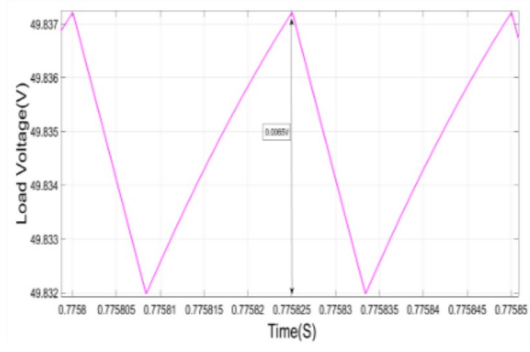


(b) figure 4

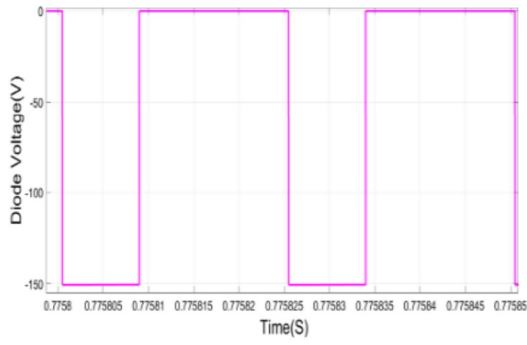


(c) figure 5

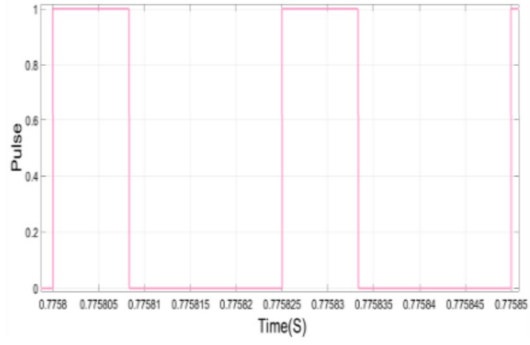


(d) figure 6

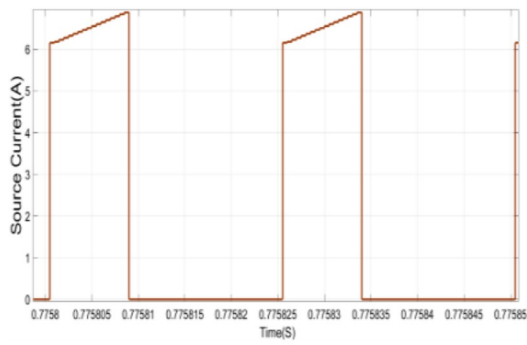


(e) figure 7

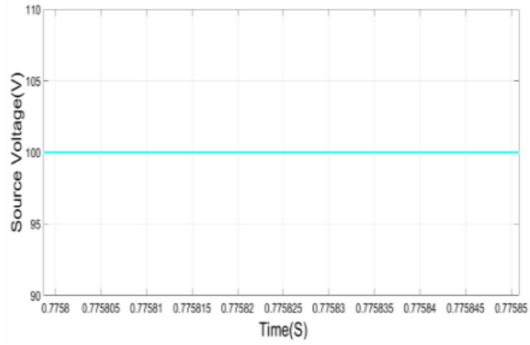

(f) figure 8

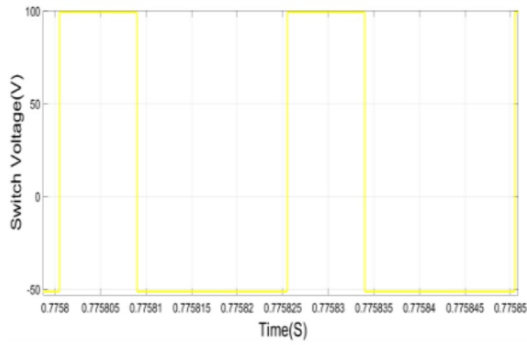


(g) figure 9

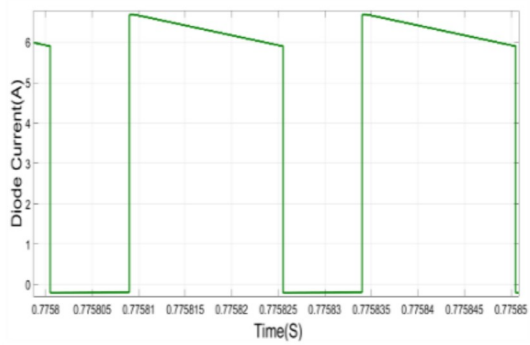

(h) figure 10

## Calculations:

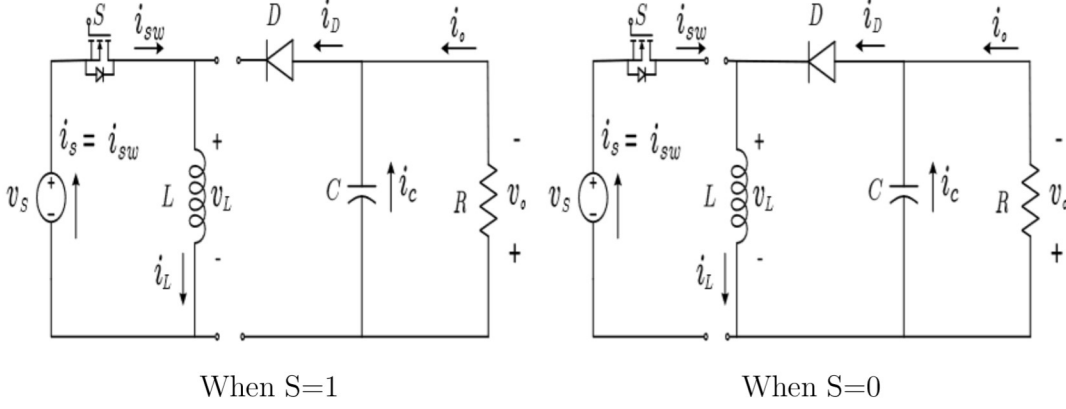

### • KVL

$$-V_{in} + V_L = 0 \quad (16)$$

$$L * \frac{\Delta I}{DT} = V_{in} \quad (17)$$

Assumed  $\Delta I = 0.8A$

$$L * \frac{0.8 * 40k}{0.333} = 100 \quad (18)$$

$$L = 1.041 \text{ mH}$$

### • KVL

$$V_L + V_o = 0 \quad (19)$$

$$L * \frac{\Delta I}{(1-D)T} = -V_o \quad (20)$$

Assumed  $\Delta I = 0.8A$

$$L * \frac{0.8 * 40K}{1 - 0.333} = -50 \quad (21)$$

$$L = 1.041 \text{ mH}$$

### • For C

$$I_o * D * T = Q = c * (\Delta V) \quad (22)$$

Assumed  $\Delta V = 0.005V$

$$C = \frac{4 * 0.333}{40K * 0.005} \quad (23)$$

$$C = 6.67 \text{ mF}$$